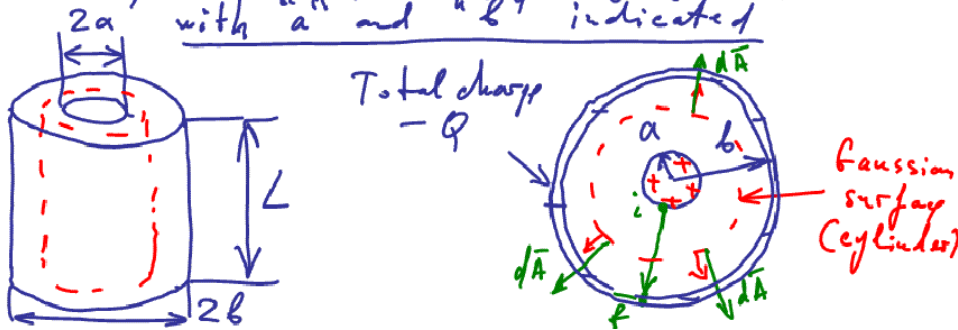


# Problem 1


Find the expression for the capacitance of an air-filled cylindrical capacitor with inner-shell radius "a" and outer-shell radius "b"

a) Sketch of the geometry of the problem with "a" and "b" indicated



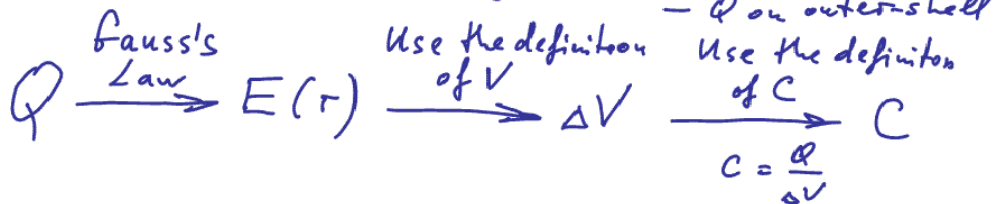b) Full sequence of steps

Assume total charge  $Q$ :  $+Q$  on inner-shell,  $-Q$  on outer-shell



c) Finding  $E(r)$

$$\Phi_e = \frac{Q_{enc}}{\epsilon_0}$$

$$\Phi_e = \oint_{\text{Gaussian surface}} \vec{E} \cdot d\vec{A} = \oint_C E(r) \cdot dA = E(r) \oint_C dA =$$

$$\vec{E} \cdot d\vec{A} = |\vec{E}| \cdot |d\vec{A}| \cdot \cos\psi = |\vec{E}| \cdot |d\vec{A}| = E(r) \cdot dA$$

$$\psi = 0^\circ \Rightarrow \cos\psi = 1$$

$$E(r) \cdot 2\pi \cdot r \cdot L$$

$Q_{enc} = Q$  - assumed charge

$$E(r) \cdot 2\pi r \cdot L = \frac{Q}{\epsilon_0} \Rightarrow E(r) = \frac{1}{2\pi\epsilon_0} \frac{Q}{r \cdot L}$$

d) Calculating  $\Delta V$

$$V_f - V_i = - \int_i^f \vec{E} \cdot d\vec{s} \text{ - definition of } V$$

$$V_f - V_i = - \int_a^b \frac{1}{2\pi\epsilon_0} \frac{Q}{r \cdot L} dr =$$

We switch from  $ds$  to  $dr$ ,  $dr = ds$

$$= - \frac{Q}{2\pi\epsilon_0 \cdot L} \int_a^b \frac{dr}{r} = - \frac{Q}{2\pi\epsilon_0 \cdot L} \ln r \Big|_a^b =$$


$$= - \frac{Q}{2\pi\epsilon_0 \cdot L} (\ln b - \ln a) = - \frac{Q}{2\pi\epsilon_0 \cdot L} \ln \frac{b}{a}$$

$$V_f - V_i < 0$$

$$\Delta V = V_i - V_f, \quad \Delta V = \frac{Q}{2\pi\epsilon_0 \cdot L} \ln \frac{b}{a}$$

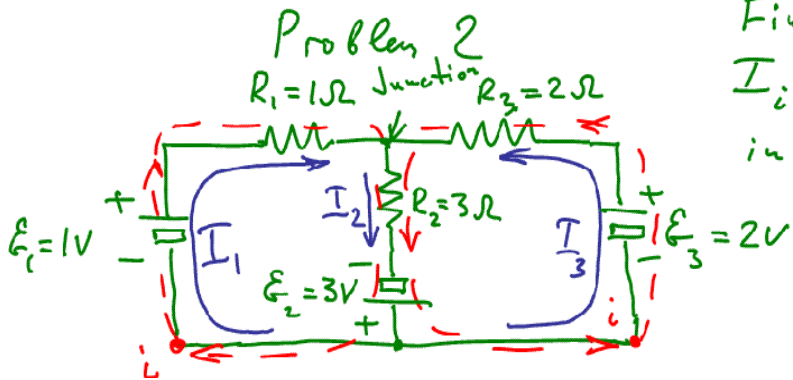e) Calculating C:

$$C = \frac{Q}{\Delta V} = \frac{\cancel{Q} \cdot 2\pi\epsilon_0 \cdot L}{\cancel{Q} \cdot \ln \frac{b}{a}} = \frac{2\pi\epsilon_0 \cdot L}{\ln \frac{b}{a}}$$



Find currents

$I_i$   $i=1,2,3$

in all  
branches

a) Sketch of the assumed directions of currents in all branches

b) Sketch of the directions of moving along the loops: clockwise or counterclockwise.

c) Equations required for solving problem for assumed directions:

$$2 - I_3 \cdot 2 - I_2 \cdot 3 + 3 = 0 \quad \text{Loop Rule (right loop)}$$

$$5 = 2I_3 + 3I_2 \quad (1)$$

$$1 - I_1 \cdot 1 - I_2 \cdot 3 + 3 = 0 \quad \text{Loop Rule (left loop)}$$

$$4 = I_1 + 3I_2 \quad (2)$$

$$I_1 + I_3 = I_2 \quad (3) \text{ - Junction Rule}$$

$$(3) \text{ in } (2): 4 = I_1 + 3(I_1 + I_3) = 4I_1 + 3I_3 \quad (4)$$

$$(3) \text{ in } (1): 5 = 2I_3 + 3(I_1 + I_3) = 3I_1 + 5I_3 \quad (5)$$

$$I_1 = \frac{5 - 5I_3}{3} = \frac{5}{3}(1 - I_3) \quad (5^*)$$

Subst. in (4)

$$4 = \frac{4 \cdot 5}{3}(1 - I_3) + 3I_3$$

$$4 = \frac{20}{3} - \frac{20}{3}I_3 + 3I_3 = \frac{20}{3} - \frac{20-9}{3}I_3 =$$

$$= \frac{20}{3} - \frac{11}{3}I_3$$

$$I_3 = \left(\frac{20}{3} - 4\right) \frac{3}{11} = \frac{20-12}{11} = \frac{8}{11} \text{ (A)}$$

From (5\*)

$$I_1 = \frac{5}{3}(1 - I_3) = \frac{5}{3}\left(1 - \frac{8}{11}\right) = \frac{5}{3} \frac{11-8}{11} =$$


$$= \frac{5}{3} \frac{3}{11} = \frac{5}{11} \text{ (A)}$$

From (3):

$$I_2 = I_1 + I_3 = \frac{8}{11} + \frac{5}{11} = \frac{13}{11} \text{ A}$$


### Problem 3

Sample problem 31-69

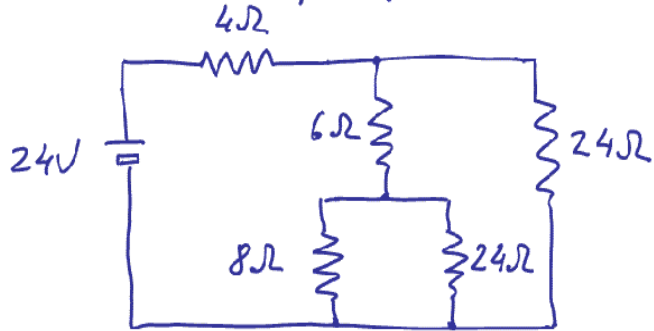


Find  $I_i$  and  $V_i$  for each resistor. Put your answers in a Table.

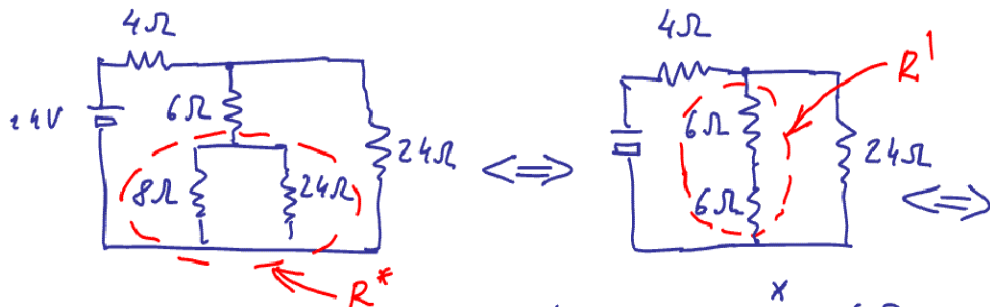- Sketch all transformations of the circuit based on the laws of series and parallel resistors
- Provide solution for each step


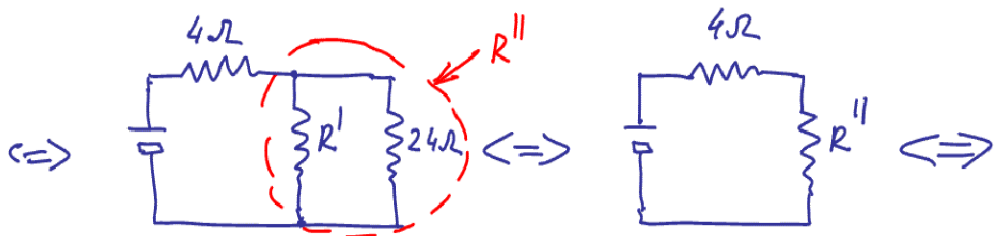
$$\frac{1}{R^*} = \frac{1}{8} + \frac{1}{24} = \frac{3+1}{24} = \frac{4}{24} = \frac{1}{6} \Rightarrow R^* = 6\Omega$$



$$R^* = 6\Omega + 6\Omega = 12\Omega$$


$$\frac{1}{R^{**}} = \frac{1}{12} + \frac{1}{24} = \frac{2+1}{24} = \frac{3}{24} = \frac{1}{8} \Rightarrow R^{**} = 8\Omega$$



We gained the value of total current  

$$I = \frac{24V}{12\Omega} = 2A$$

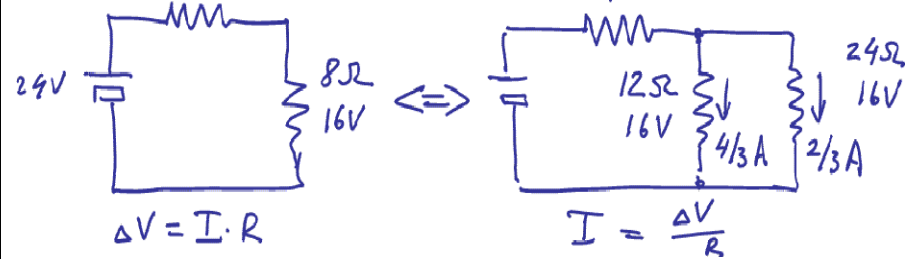As we rebuild the circuit, we note that series resistors must have the same current and the parallel resistors must have the same  $\Delta V$ .  
 $4\Omega, 8V$        $4\Omega, 8V$




**Step 1**  
 The  $12\Omega$  resistor is returned to  $4\Omega$  and  $8\Omega$  resistors in series. Both resistors must have the same  $2.0A$  current as the  $12\Omega$  resistor

**Step 2**  
 The  $8\Omega$  resistor is returned to the  $12\Omega$  and  $24\Omega$  resistors in parallel. Both resistors must have the same  $\Delta V = 16V$  as the  $8\Omega$  resistor. From Ohm's law,  

$$I_{12} = (16V)/(12\Omega) = \frac{4}{3}A$$
  

$$I_{24} = \frac{2}{3}A$$

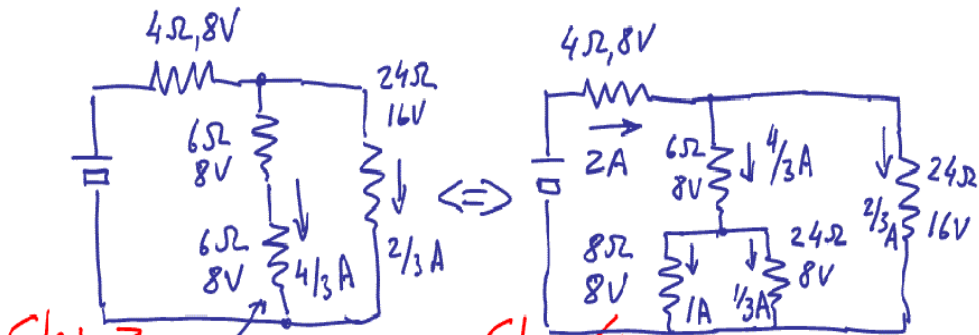

**Step 3**  
 12Ω resistor is returned to the two 6Ω resistors in series. Both resistors must have the same  $\frac{4}{3}A$  as the 12Ω resistor. Due to Ohm's law their  $\Delta V_6 = I \cdot R = 8V$  for each resistor


**Step 4**  
 The 6Ω resistor is returned to the 8Ω and 24Ω resistors in parallel. Both resistors must have the same  $\Delta V = 8V$  as the 6Ω resistor. From Ohm's law  $I_8 = (8V)/(8\Omega) = 1A$  and  $I_{24} = \frac{1}{3}A$ .

Table of answers

Resistor	Potential Difference $\Delta V (V)$	Current (A)
4Ω	8	2
6Ω	8	$\frac{4}{3}$
8Ω	8	1
Bottom 24Ω	8	$\frac{1}{3}$
Right 24Ω	16	$\frac{2}{3}$

### Problem 4

Sample problem 31-77

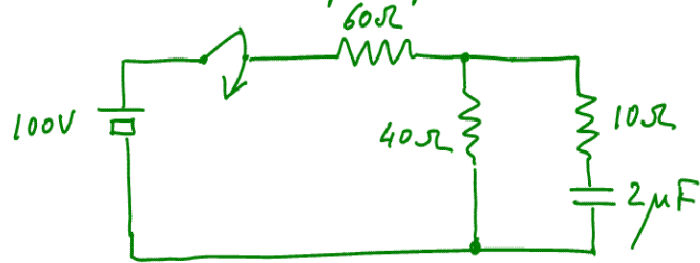

The switch has been closed for a long time


a) What is the charge  $Q_c^-$ ?

b) The switch is opened at  $t = 0s$

At what time has the charge on the capacitor decreased to 10% of its initial value?

Understanding of the steady state of the circuit with the switch being closed for a long time.

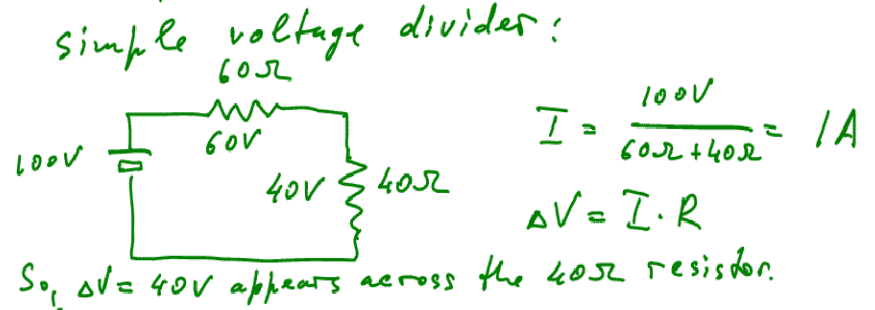The capacitor is fully charged and there is no current in the right branch that contains C. So, the capacitor can be modeled as a break, and the circuit becomes to be a simple voltage divider:



This voltage is applied to the capacitor.

So, the charge on the capacitor is

$$Q_0 = (\Delta V) \cdot C = (40V) \cdot (2 \cdot 10^{-6} F) = 80 \mu C$$

### Mathematical description of the transient process occurring after opening the switch

Once the switch is opened, the battery is disconnected. The capacitor  $C$  has two resistors ( $10 \Omega$  and  $40 \Omega$ ) in series and discharges according to

$$Q_C = Q_0 \cdot e^{-\frac{t}{\tau}}, \quad \text{where } \tau = RC$$

$R = 10 \Omega + 40 \Omega = 50 \Omega$

$$\tau = 50 \Omega \cdot 2 \cdot 10^{-6} F = 100 \cdot 10^{-6} s = 0.1 \text{ ms}$$

For  $Q = 0.1 \cdot Q_0$

$$0.1 \cdot Q_0 = Q_0 \cdot e^{-\frac{t}{\tau}} \Rightarrow 0.1 = e^{-\frac{t}{\tau}}$$

$$\ln 0.1 = -\frac{t}{\tau}$$

$$-2.3 = -\frac{t}{\tau} \Rightarrow t = 2.3 \cdot \tau = \underline{\underline{0.23 \text{ ms}}}$$